
 


From NAND to Tetris

 Building a Modern Computer From First Principles



Home
Prerequisites
Syllabus
Course
Book
Software
Terms
Papers
Talks
Cool Stuff
About
Team
Q&A

Project 3: Sequential Chips

Background

The computer's main memory, also called *Random Access Memory*, or *RAM*, is an addressable sequence of n -bit registers, each designed to hold an n -bit value. In this project you will gradually build a RAM unit. This involves two main issues: (i) how to use gate logic to store bits persistently, over time, and (ii) how to use gate logic to locate ("address") the memory register on which we wish to operate.

Objective

Build all the chips described in Chapter 3 (see list below), leading up to a *Random Access Memory* (RAM) unit. The only building blocks that you can use are primitive DFF gates, chips that you will build on top of them, and chips described in previous chapters.

Chips

Chip (HDL)	Description	Test script	Compare file
DFF	Data Flip-Flop (primitive)		
Bit	1-bit register	Bit.tst	Bit.cmp
Register	16-bit register	Register.tst	Register.cmp
RAM8	16-bit / 8-register memory	RAM8.tst	RAM8.cmp
RAM64	16-bit / 64-register memory	RAM64.tst	RAM64.cmp
RAM512	16-bit / 512-register memory	RAM512.tst	RAM512.cmp
RAM4K	16-bit / 4096-register memory	RAM4K.tst	RAM4K.cmp
RAM16K	16-bit / 16384-register memory	RAM16K.tst	RAM16K.cmp
PC	16-bit program counter	PC.tst	PC.cmp

Contract

When loaded into the supplied *Hardware Simulator*, your chip design (modified .hdl program), tested on the supplied .tst script, should produce the outputs listed in the supplied .cmp file. If that is not the case, the simulator will let you know.

Resources

The relevant reading for this project is [Chapter 3](#) and [Appendix A](#). Specifically, all the chips described in Chapter 3 should be implemented in the *Hardware Description Language* (HDL) specified in Appendix A.

For each chip, we supply a skeletal .hdl file with a missing implementation part. In addition, for each chip we supply a .tst script that instructs the hardware simulator how to test it, and a .cmp ("compare file") containing the correct output that this test should generate. Your job is to complete and test the supplied skeletal .hdl files.

The resources that you need for this project are the supplied *Hardware Simulator* and the files listed above. If you've downloaded the *Nand2Tetris Software Suite*, these files are stored in your projects/03 directory. The directory is further partitioned into two sub-directories, for reasons described below.

Tips

The Data Flip-Flop (DFF) gate is considered primitive and thus there is no need to build it: when the simulator encounters a DFF chip part in an HDL program, it automatically invokes the built-in tools/builtInChips/DFF.hdl implementation.

Built-in chips: When constructing RAM chips from lower-level RAM chip-parts, we recommend using built-in versions of the latter. Otherwise, the simulator will recursively generate numerous memory-resident software objects, one for each one of the many chip parts that make up a typical RAM unit. This may cause the simulator to run slowly, or, worse, out of memory. i.e. out of the memory of the computer on which the simulator is running.

To avert this problem, we've partitioned the RAM chips that you have to build in this project into two sub-directories, named projects/03/a and projects/03/b. This partition is superficial, and is done with one purpose only: when building the chips stored in b, the simulator is forced to use built-in implementations of the lower-level chip parts whose .hdl programs are stored in a but not in b.

Tools

All the chips mentioned projects 0-5 can be implemented and tested using the supplied *Hardware Simulator*. Here is a screen shot of testing a built-in RAM8.hdl chip implementation on the Hardware Simulator:

Input pins

Name	Value
in[16]	112
load	1
address[3]	5

Output pins

Name	Value
out[16]	

RAM 8

Address	Value
0	0
1	0
2	0
3	0
4	0
5	0
6	0
7	0

HDL

```

* In words: the chip always outputs
* location specified by address. If
* into the memory location specifi
* available through the out output
*/

CHIP RAM8 {
    IN in[16], load, address[3];
    OUT out[16];

    BUILTIN RAM8;
    CLOCKED in, load;
}
  
```

Annotations:

- GUI of the loaded built-in chip**: Points to the top toolbar area.
- The user enters some input values and clicks the clock icon to pace the clock. Each click generates a tick or a tock. The clock can also be paced using a test script.**: Points to the 'Input pins' table.
- A built-in RAM8 chip is loaded**: Points to the HDL code editor.

Text Box:

Clocked (sequential) chips are *clock-dependent*.

Therefore, the standard way to test a clocked chip is to set its input pins to some values (as with combinational chips), simulate the progression of the clock, and watch how the chip logic responds to the clock's ticks and tocks.

This screen shot illustrates the simulation of a built-in 8-word random-access memory chip (RAM8).