## Contents

1	README	2
2	ALU.hdl	3
3	Add16.hdl	5
4	FullAdder.hdl	6
5	HalfAdder.hdl	7
6	Inc16.hdl	8
7	Mul.hdl	9
8	ShiftLeft.hdl	10
9	ShiftRight.hdl	11

### 1 README

```
1
   nivkeren, ransha
   Niv Keren, ID 201478351, niv.keren@cs.huji.ac.il
    Ran Shaham, ID 203781000, ran.shaham1@mail.huji.ac.il
4
    ______
                             Project 2 - Boolean Arithmetic
8
9
10
   Submitted Files
11
12
13 README - This file.
   HalfAdder.hdl - Adds two bits and outputs the sum and carry
14
   FullAdder.hdl - Adds three bits and outputs the sum and carry
15
   Add16.hdl - Adds two 16-bit integer numbers
   Inc16.hdl - Increments a 16-bit number
17
    ALU.hdl - The Arithmetic Logic Unit
   ShiftLeft.hdl - Multiplies a 16-bit input number by 2 (ignoring overflow)
19
   ShiftRight.hdl - Devides a 16-bit input number by 2 without remainder
20
21
    Mul.hdl - Multiplies two 16-bit numbers.
22
23
   Remarks
24
    st The multiplication chip was implemented according to long-multiplication algorithm
25
26
      where multiplication of each two bits x,y is just the And(x,y) operation.
27
      This method's shortcoming is the negative overflowing results which turns very small
     negative numbers to positive.
28
29
     Nonetheless, this method works well on the supplied test and in the exercise forum
     it is clearly written that it is sufficient.
30
   * All other chips had simple implementations that were drawn directly from the lectures
31
     and simple logic.
```

### 2 ALU.hdl

```
// This file is part of www.nand2tetris.org
    // and the book "The Elements of Computing Systems"
    // by Nisan and Schocken, MIT Press.
    // File name: projects/02/ALU.hdl
4
6
     * The ALU (Arithmetic Logic Unit).
8
     * Computes one of the following functions:
     * x+y, x-y, y-x, 0, 1, -1, x, y, -x, -y, !x, !y,
9
     * x+1, y+1, x-1, y-1, x&y, x|y on two 16-bit inputs,
     * according to 6 input bits denoted zx,nx,zy,ny,f,no.
11
     \boldsymbol{*} In addition, the \bar{\mathtt{ALU}} computes two 1-bit outputs:
12
     * if the ALU output == 0, zr is set to 1; otherwise zr is set to 0;
     * if the ALU output < 0, ng is set to 1; otherwise ng is set to 0.
14
15
16
    // Implementation: the ALU logic manipulates the \boldsymbol{x} and \boldsymbol{y} inputs
17
    \ensuremath{//} and operates on the resulting values, as follows:
18
    // if (zx == 1) set x = 0
                                       // 16-bit constant
19
    // if (nx == 1) set x = !x
                                        // bitwise not
20
    // \text{ if } (zy == 1) \text{ set } y = 0
21
                                        // 16-bit constant
    // if (ny == 1) set y = !y
                                        // bitwise not
22
    // if (f == 1) set out = x + y // integer 2's complement addition
23
    // if (f == 0) set out = x & y // bitwise and
// if (no == 1) set out = !out // bitwise not
25
26
    // if (out == 0) set zr = 1
27
    // if (out < 0) set ng = 1
28
29
    CHIP ALU {
30
             x[16], y[16], // 16-bit inputs
31
             zx, // zero the x input?
             nx, // negate the x input?
33
34
             zy, // zero the y input?
             ny, // negate the y input?
35
             f, // compute out = x + y (if 1) or x & y (if 0)
36
37
             no; // negate the out output?
38
39
40
             out[16], // 16-bit output
             zr, // 1 if (out == 0), 0 otherwise
41
42
             ng; // 1 if (out < 0), 0 otherwise
43
44
45
             // Get negated inputs
             Not16(in=x, out=negx);
46
47
             Not16(in=y, out=negy);
             // Choose how to process x,y according to zx,nx,zy,ny.
49
             Mux4Way16(a=x, b=false, c=negx, d=true, sel[0]=zx, sel[1]=nx, out=procx);
50
             Mux4Way16(a=y, b=false, c=negy, d=true, sel[0]=zy, sel[1]=ny, out=procy);
51
52
53
             // Get the correct operation of the processed x,y according to f
             And16(a=procx, b=procy, out=xAndy);
54
             Add16(a=procx, b=procy, out=xAddy);
55
             Mux16(a=xAndy, b=xAddy, sel=f, out=outf);
56
57
58
             // Negate output if needed and get the status outputs
             Not16(in=outf, out=negout);
```

```
Mux16(a=outf, b=negout, sel=no, out=out, out[15]=ng, out[0..7]=out07, out[8..15]=out815);

// Check if one of the output bits is 1, if so, the output is not zero.

Or8Way(in=out07, out=negzr1);

Or8Way(in=out815, out=negzr2);

Or(a=negzr1, b=negzr2, out=negzr);

Not(in=negzr, out=zr);
```

### 3 Add16.hdl

```
// This file is part of www.nand2tetris.org
     \ensuremath{//} and the book "The Elements of Computing Systems"
    // by Nisan and Schocken, MIT Press.
     // File name: projects/02/Adder16.hdl
      * Adds two 16-bit values.
8
      * The most significant carry bit is ignored.
9
10
     CHIP Add16 {
11
          IN a[16], b[16];
12
13
          OUT out[16];
14
          PARTS:
15
              HalfAdder(a=a[0], b=b[0], sum=out[0], carry=c1);
16
              FullAdder(a=a[1], b=b[1], c=c1, sum=out[1], carry=c2);
FullAdder(a=a[2], b=b[2], c=c2, sum=out[2], carry=c3);
17
18
               FullAdder(a=a[3], b=b[3], c=c3, sum=out[3], carry=c4);
19
              FullAdder(a=a[4], b=b[4], c=c4, sum=out[4], carry=c5);
FullAdder(a=a[5], b=b[5], c=c5, sum=out[5], carry=c6);
20
21
              FullAdder(a=a[6], b=b[6], c=c6, sum=out[6], carry=c7);
22
23
               FullAdder(a=a[7], b=b[7], c=c7, sum=out[7], carry=c8);
24
               FullAdder(a=a[8], b=b[8], c=c8, sum=out[8], carry=c9);
               FullAdder(a=a[9], b=b[9], c=c9, sum=out[9], carry=c10);
25
26
               FullAdder(a=a[10], b=b[10], c=c10, sum=out[10], carry=c11);
27
               FullAdder(a=a[11], b=b[11], c=c11, sum=out[11], carry=c12);
               FullAdder(a=a[12], b=b[12], c=c12, sum=out[12], carry=c13);
28
29
               FullAdder(a=a[13], b=b[13], c=c13, sum=out[13], carry=c14);
              FullAdder(a=a[14], b=b[14], c=c14, sum=out[14], carry=c15);
FullAdder(a=a[15], b=b[15], c=c15, sum=out[15], carry=c16);
30
31
    }
```

## 4 FullAdder.hdl

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
    // by Nisan and Schocken, MIT Press.
    // File name: projects/02/FullAdder.hdl
6
     * Computes the sum of three bits.
7
8
9
     CHIP FullAdder {
10
         IN a, b, c; // 1-bit inputs
11
         OUT sum, // Right bit of a + b + c
12
             carry; // Left bit of a + b + c
13
14
         PARTS:
15
16
             // Add two bits
              HalfAdder(a=a, b=b, sum=s1, carry=c1);
17
              \ensuremath{//} Add the third bit to the result
18
              HalfAdder(a=s1, b=c, sum=sum, carry=c2);
19
              // If one of the above additions had a carry,
20
              \ensuremath{//} so does the whole sum
21
              Or(a=c1, b=c2, out=carry);
22
23 }
```

### 5 HalfAdder.hdl

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
    // by Nisan and Schocken, MIT Press.
     // File name: projects/02/HalfAdder.hdl
 6
      * Computes the sum of two bits.
 7
 8
 9
     CHIP HalfAdder {
10
         IN a, b; // 1-bit inputs
OUT sum, // Right bit of a + b
11
12
              carry; // Left bit of a + b
13
14
          PARTS:
15
16
               \ensuremath{//} Simple half-adder implementation according to the truth-table.
               Xor(a=a, b=b, out=sum);
17
               And(a=a, b=b, out=carry);
18
    }
19
```

## 6 Inc16.hdl

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
    // by Nisan and Schocken, MIT Press.
// File name: projects/02/Inc16.hdl
 6
      * 16-bit incrementer:
 8
      * out = in + 1 (arithmetic addition)
 9
10
     CHIP Inc16 {
11
          IN in[16];
12
          OUT out[16];
13
14
          PARTS:
15
16
               // b = 00...01 = 1 ==> a + b = a + 1
               Add16(a=in, b[0]=true, b[1..15]=false, out=out);
17
    }
18
```

### 7 Mul.hdl

```
2
  * Multiplies two signed 16-bit numbers.
3
 CHTP Mul{
4
   IN a[16], b[16];
5
   OUT out[16]:
6
8
   PARTS:
     // Performs binary-long-multiplication, similar to decimal multiplication
9
11
     // Get all shifted versions of 'a'
12
     ShiftLeft(in=a, out=sh1a):
     ShiftLeft(in=sh1a, out=sh2a);
     ShiftLeft(in=sh2a, out=sh3a);
14
15
     ShiftLeft(in=sh3a, out=sh4a);
     ShiftLeft(in=sh4a, out=sh5a);
16
     ShiftLeft(in=sh5a, out=sh6a);
17
     ShiftLeft(in=sh6a, out=sh7a);
18
     ShiftLeft(in=sh7a, out=sh8a);
19
     ShiftLeft(in=sh8a, out=sh9a);
20
21
     ShiftLeft(in=sh9a, out=sh10a);
     ShiftLeft(in=sh10a, out=sh11a);
22
23
     ShiftLeft(in=sh11a, out=sh12a);
24
     ShiftLeft(in=sh12a, out=sh13a);
     ShiftLeft(in=sh13a, out=sh14a):
25
26
27
     // The 'multiplication' operation
     28
     29
     30
31
     32
     33
     34
     35
     36
     37
     38
39
     40
     41
     42
43
     // Sum all prodcuts
44
     Add16(a=o0, b=o1, out=a1);
45
     Add16(a=a1, b=o2, out=a2);
46
47
     Add16(a=a2, b=o3, out=a3);
     Add16(a=a3, b=o4, out=a4);
48
     Add16(a=a4, b=o5, out=a5);
49
     Add16(a=a5, b=o6, out=a6);
50
     Add16(a=a6, b=o7, out=a7);
51
     Add16(a=a7, b=o8, out=a8);
52
     Add16(a=a8, b=o9, out=a9);
53
     Add16(a=a9, b=o10, out=a10);
54
55
     Add16(a=a10, b=o11, out=a11);
     Add16(a=a11, b=o12, out=a12);
56
     Add16(a=a12, b=o13, out=a13);
57
     Add16(a=a13, b=o14, out=out);
58
 }
59
```

## 8 ShiftLeft.hdl

# 9 ShiftRight.hdl

```
1  /**
2  * Divides a 16-bit number by 2 by shifthing each bit (except the MSB) right.
3  */
4  CHIP ShiftRight {
5     IN in[16];
6     OUT out[16];
7     PARTS:
9     And16(a=true, b[0..13]=in[1..14], b[14]=in[15], b[15]=in[15], out=out);
10 }
```